



TECHNO INDIA NJR INSTITUTE OF TECHNOLOGY

Name Dhruv Bagora Branch CSE Sem 1st
Roll No. _____ Date _____

EXPERIMENT - 5

Objective - Study of single phase half wave uncontrolled rectifier.

- (1) Explain rectification.
- (2) Explain Half wave rectification.
- (3) Explain Half wave rectification: For +ve half cycle.
- (4) Explain Half wave rectification: For -ve half cycle.

Apparatus Required - AC source, Resistive load, diode.

• Rectification -

Alternating current \rightarrow Rectifier \rightarrow Direct current


A rectifier is a device that converts alternating current (AC) to direct current (DC), a process known as rectification. Rectifiers are essentially of two types - a half wave rectifier and a full wave rectifier.

• Half Wave Rectification -



On the positive cycle the diode is forward biased.

By using a diode we have converted an AC source into a pulsating DC source. In summary we have "rectified" the AC signal.

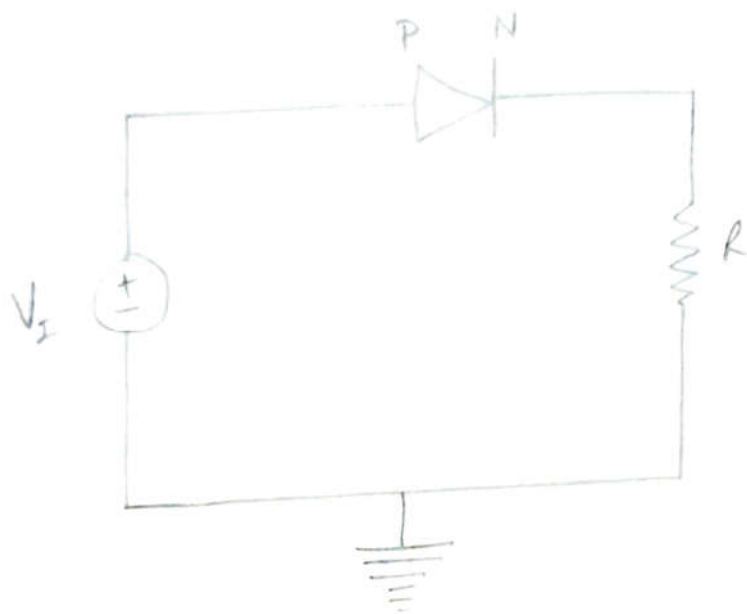The simplest kind of rectifier circuit is the half wave rectifier. The half wave rectifier is a circuit that allows only part of an input signal to pass.



Half Wave Rectifiers - Waveforms

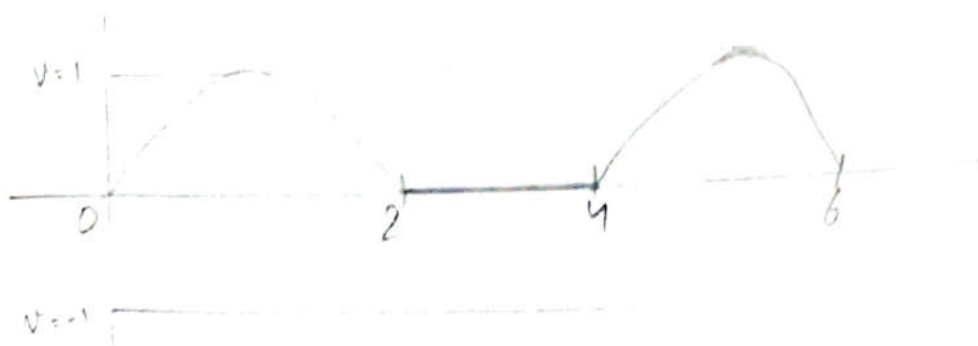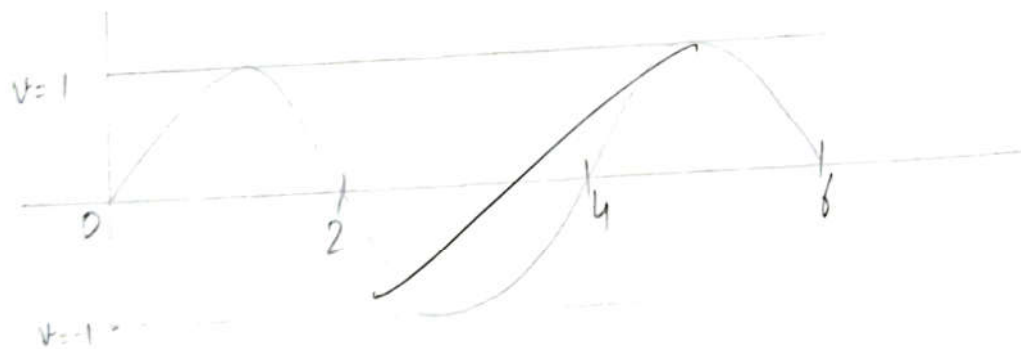



TECHNO INDIA NJR INSTITUTE OF TECHNOLOGY

Name Dhrum Bagaria Branch CSE Sem 1st
Roll No. _____ Date _____

The circuit is simply the combination of a signal diode in series with a resistor, where the resistor is acting as a load.

- Half wave Rectifiers -

The output DC voltage of a half wave rectifier can be calculated with the following two ideal equations.

$$V_{peak} = V_{rms} \times \sqrt{2}$$

$$V_{ac} = \frac{V_{peak}}{\pi}$$

where, V_i = Input voltage
 V_b = bar




- Half wave Rectification - For +ve half cycle :
Diode is forward biased, acts as a short circuit passes the waveform through.
For +ve half cycle :

$$V_i - V_b - I R_d - I R = 0$$

where, V_i = input voltage
 V_b = barrier potential
 R_d = diode resistance
 I = total current
 R = resistance

$$I = \frac{V_i - V_b}{R_d + R}$$

for a more accurate DI,

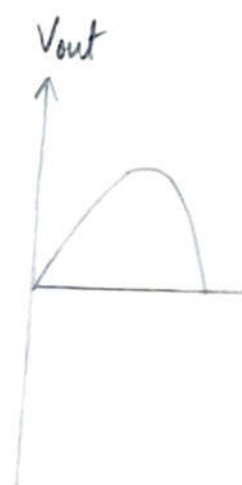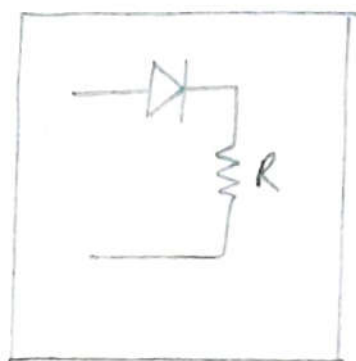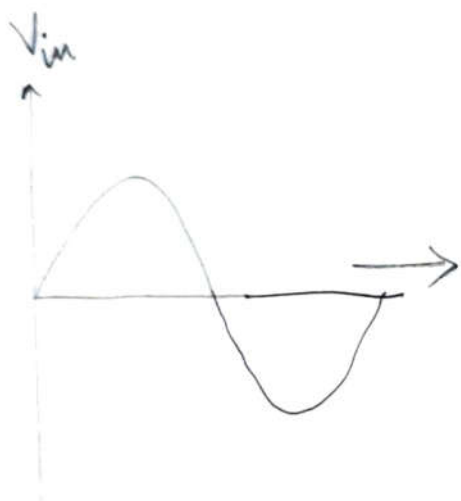



TECHNO INDIA NJR INSTITUTE OF TECHNOLOGY

Name Dhruv Bagora Branch CSE Sem 1st
Roll No. _____ Date _____

$$V_o = IR$$

$$V_o = \frac{V_I - V_b}{r_d + R} \times R$$

for $r_d \ll R$

$$V_o = V_I - V_b$$

V_b is 0.3 for germanium.

V_b is 0.7 for silicon.

• For $V_I < V_b$:

The diode will remain off. The output voltage will be

$$V_o = 0$$

• For $V_I > V_b$:

The diode will remain on. The output voltage will be,

$$V_o = V_I - V_b$$

Average output voltage -

$$V_o = V_m \sin \omega t$$

$$\forall 0 \leq \omega t \leq \pi$$

$$V_o = 0$$

$$\forall \pi \leq \omega t \leq 2\pi$$

$$V_{av} = \frac{V_m}{\pi} = 0.318 V_m$$

Observation Table -

Max. Input V	Theoretical V_{rms}	Practical V_{rms}
10V	5V	5.09V

Calculations -

$$\text{diff. percentage} = \frac{| \text{practical} - \text{Theo.} |}{\text{Theo.}} \times 100$$

$$= \frac{| 5.09 - 5 |}{5} \times 100$$

$$= \underline{\underline{18\%}}$$



TECHNO INDIA NJR INSTITUTE OF TECHNOLOGY

Name Dhruv Bagora Branch CSE Sem 1st
Roll No. _____ Date _____

- RMS load voltage -

$$V_{rms} = I_{rms} R = \frac{V_m}{2}$$

- Average load current -

$$I_{av} = \frac{V_{av}}{R} = \frac{\frac{V_m}{\pi}}{R}$$

$$I_{av} = \frac{V_m}{\pi R} = \frac{I_m}{\pi}$$

- RMS load current

$$I_{rms} = \frac{I_m}{2}$$

- Form factor - It is defined as the ratio of rms load voltage and average load voltage

$$F.F. = \frac{V_{rms}}{V_{av}}$$

$$F.F. = \frac{\frac{V_m}{2}}{\frac{V_m}{\pi}} = \frac{\pi}{2} = 1.57$$

$$F.F. \geq 1$$

$$I_{rms} \geq I_{av}$$

for a sine wave duration πT



TECHNO INDIA NJR INSTITUTE OF TECHNOLOGY

Name Shruv Bagora Branch CSE Sem 1st
Roll No. _____ Date _____

• Ripple Factor -

$$\gamma = \sqrt{F.F^2 - 1} \times 100\%$$

$$\gamma = \sqrt{1.57^2 - 1} \times 100\%$$

$$\gamma = \underline{1.21\%}$$

• Efficiency - It is defined as the ratio of dc power available at the load to the input ac power

$$\eta\% = \frac{P_{\text{load}}}{P_{\text{in}}} \times 100\%$$

$$\eta\% = \frac{I_{\text{dc}}^2 \times R}{I_{\text{rms}}^2 \times R} \times 100\%$$

$$\eta\% = \frac{\frac{I_m^2}{\pi^2}}{\frac{I_m^2}{4}} \times 100\%$$

$$\eta\% = \frac{4}{\pi^2} \times 100$$

$$= \underline{40.56\%}$$

Result - we have studied a single phase Half wave rectifier and wave forms are shown.

Shruv
24/01/22 & H