
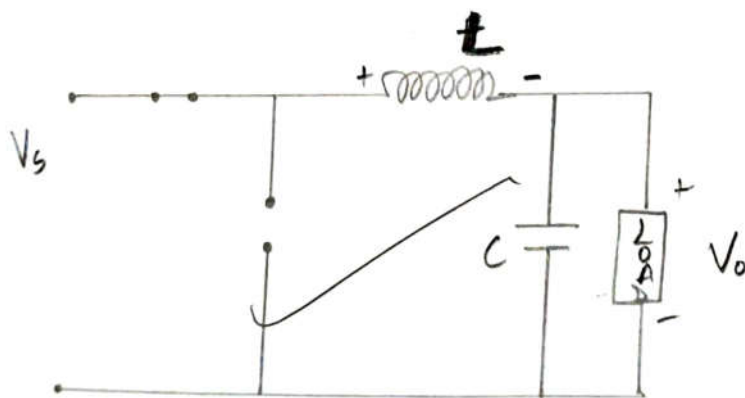


(i) Switch ON

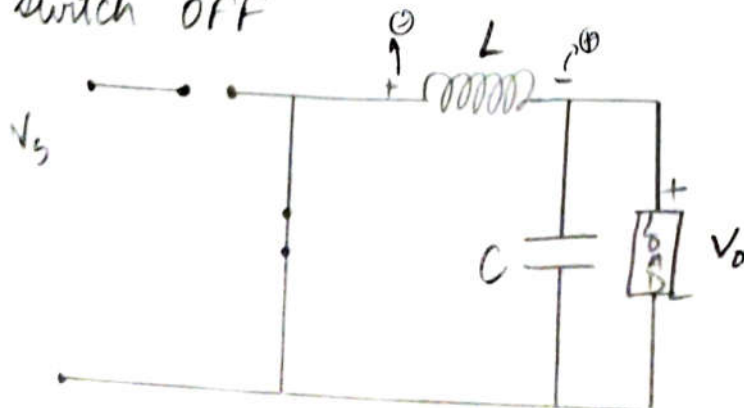

(ii) Switch OFF





# TECHNO INDIA NJR INSTITUTE OF TECHNOLOGY

Name Dheeraj Bagoria Branch CSE Sem 1<sup>st</sup>  
Roll No. \_\_\_\_\_ Date \_\_\_\_\_

## EXPERIMENT 9

Objective - Study of DC-DC Buck converter with R load and observed effect of duty ratio on converter output voltage.

Apparatus Required - DC-DC Buck converter, trainer kit, two channel DSO, connection leads.

Theory -


Circuit description -

The three basic dc-dc converter use a pair of switches, usually one controlled (eg. MOSFET) and one uncontrolled (i.e., diode), to achieve unidirectional power flow from input to output. The converters also use one capacitor and one inductor to store and transfer energy from input to output. They also filter or smooth voltage and current.

The dc-dc converters can have two distinct modes of operation: Continuous conduction mode (CCM) and discontinuous conduction mode (DCM). In practice, a converter may operate in both modes, which have significantly diff. characteristics. Therefore, a converter and its control should be designed based on both modes of operation. However, for this course we only consider the dc-dc converters operated in CCM.

Circuit operation -

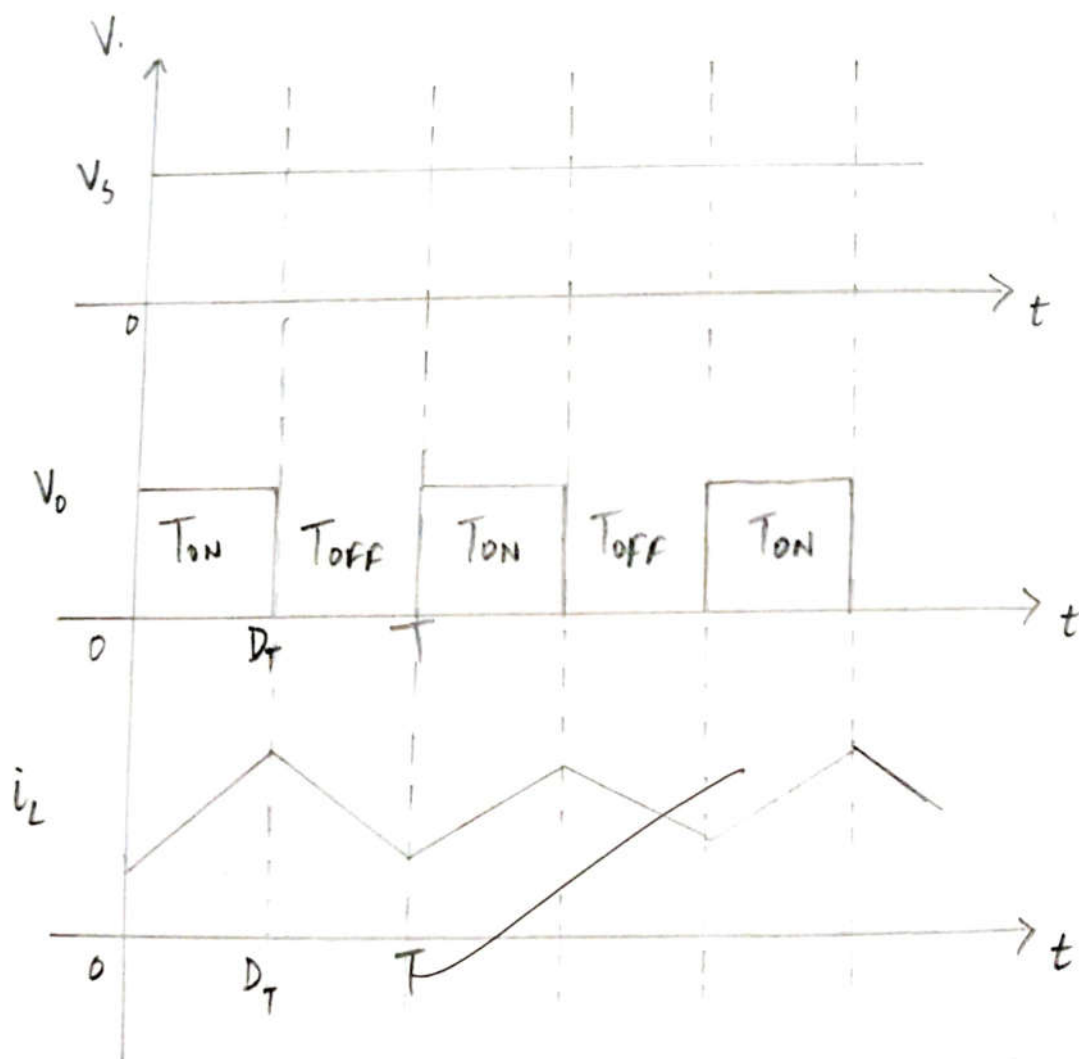When the switch is on for a time duration  $DT$ ,



waveforms





# TECHNO INDIA NJR INSTITUTE OF TECHNOLOGY

Name Dhruv Bagora Branch CSE Sem 1<sup>st</sup>  
Roll No. \_\_\_\_\_ Date \_\_\_\_\_

the switch conducts the inductor current and the diode becomes reverse biased. This results in a +ve voltage  $V_L = V_s - V_o$  across the inductor. This voltage causes a linear increase in the inductor current  $i_L$ . When the switch is turned off, because of the inductive energy storage,  $i_L$  continues to flow. This current now flows through the diode, and  $V_L = -V_o$  for a time duration  $(1-D)T$  until the switch is turned on again.

• Volt second Balance equation -

Voltage upto time  $DT = V_s - V_o$

Voltage for time  $(T-DT) = 0 - V_o = -V_o$

$$\frac{(V_s - V_o) DT}{K} = - \left( \frac{-V_o}{K} \right) T(1-D)$$

$$V_s D - V_o D = V_o - V_o D$$

$$\boxed{V_o = V_s D} \quad \text{volt second balance eq}^n$$

$V_o$  = output voltage

$V_s$  = input voltage

$D$  = Duty ratio / Duty cycle =  $\frac{T_{on}}{T} = \frac{T_{on}}{T_{on} + T_{off}}$

Observation Table -

Sr.No.	Input voltage ( $V_s$ )	Duty Ratio ( $D$ )	Output voltage ( $V_o$ )
1.	24V	15%	5.20V
2.	24V	20%	7.2V
3.	24V	30%	10.4V
4.	24V	40%	12.8V
5.	24V	50%	14.8V
6.	24V	60%	16V
7.	24V	70%	17.2V
8.	24V	80%	18.4V
9.	24V	90%	20.4V
10.	24V	95%	21.6V

For  $R_L = 36.6 \Omega$   
 Frequency = 2 KHz.



# TECHNO INDIA NJR INSTITUTE OF TECHNOLOGY

Name Dhruv Bagora Branch CSE Sem 1<sup>st</sup>  
Roll No. \_\_\_\_\_ Date \_\_\_\_\_

Result - We have studied and observed the DC-DC buck converter with R load and observed effect of duty ratio on converted output voltage.

✓ Aheer  
25/1/22

\*\*\*